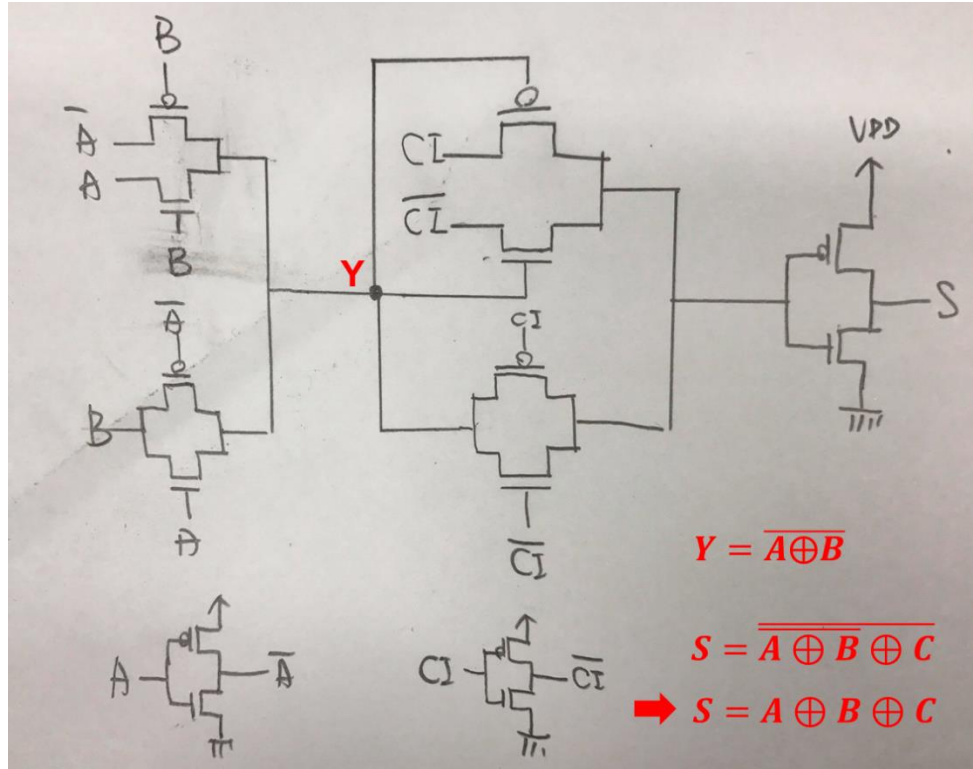



HW2 參考解答

1.(70%, each for 35%) 這邊舉 FA1 圖的右半部為例(Sum)

Transistor-level (10%)



Gate-level circuit (1%)

 

Truth table (5%)



| A | B | CI | S |
|---|---|----|---|
| 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 1 |
| 0 | 1 | 0 | 1 |
| 0 | 1 | 1 | 0 |
| 1 | 0 | 0 | 1 |
| 1 | 0 | 1 | 0 |
| 1 | 1 | 0 | 0 |
| 1 | 1 | 1 | 1 |

Waveform (10%) Code (4%) Discuss problems you have encountered. (5%)

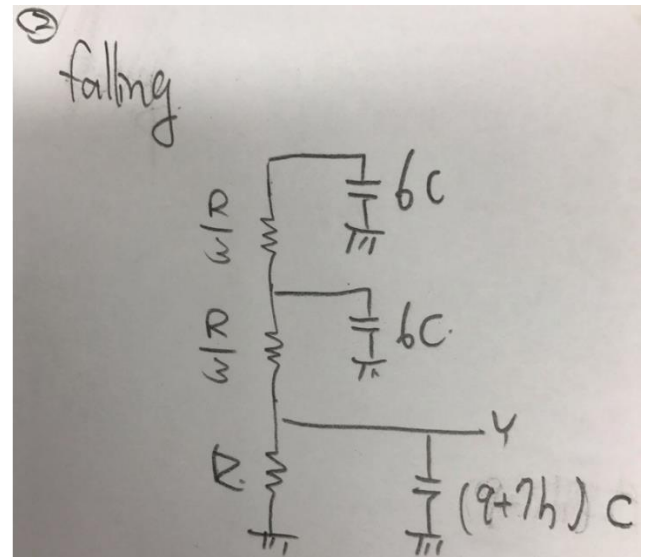 2. (20%)

Rising delay (10%) Falling delay (10%)

等效電路圖如下，使用 Elmore delay model 來求出 rising & falling delay



3. (10%)

Dynamic power (5%, reason for 4%)

Static power (5%, reason for 4%)

$V_{DD} \downarrow$, Due to $P_{sw} = \alpha C V_{DD}^2 f$, Dynamic power \downarrow

To maintain clock speed , we will to reduce V_t , but the leakage current will increase .

So the P_{static} will \uparrow